

ELEC 344 - 101: Applied Electronics and Electromechanics

Instructor: Ignacio Galiano Zurbriggen

TAs:

Gabriel Ferreira (gabriel@ece.ubc.ca)

Jorge May (jorgemay@ece.ubc.ca)

Daniel Hsu (danielhsu@ece.ubc.ca)

Lucas Sinopoli (sinopoli@ece.ubc.ca)

Tania Mair (mairgarc@student.ubc.ca)

Assignment 1

Due February 12th, 11:59 pm.

Submit through Canvas

(Submit a typed report, include the procedure and steps followed to reach the results.

Long derivations can be included in a non-typed appendix.)

- 1) Using the circuit in Fig. 1:
 - a) Solve the circuit and find the voltage V_X .
 - b) Add a capacitor of $100\ \mu\text{F}$ in parallel with R_3 and find the equivalent RC circuit (Thevenin).
 - c) Find the expression for the capacitor voltage and calculate the time constant for charging the capacitor.
 - d) Run the simulation in PSIM. Show the relevant waveforms during the capacitor charging transient.

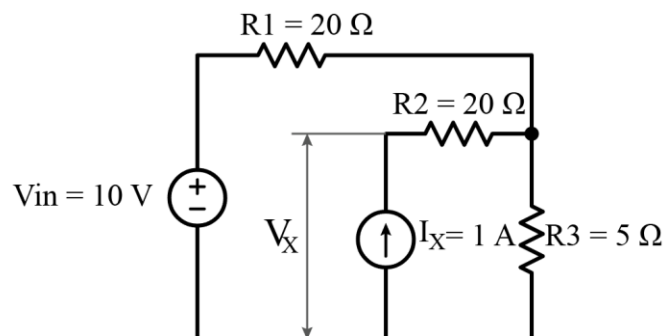


Fig. 1 – DC Circuit

- 2) Using the circuit in Fig. 2 with an input power supply $v_{in} = \sqrt{2} \ 110 \sin(\omega t)$ V, and $f = 60$ Hz
- Calculate magnitude and phase of the input current.
 - Add a capacitor in parallel with the inductor. Calculate the value of the capacitor to obtain a 0 degree phase shift between input current and voltage.

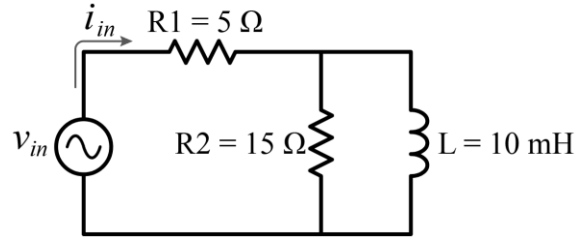


Fig. 2 – AC Circuit

- 3) Fig. 3 illustrates an ideal 3-Phase rectifier with the following parameters:

- $v_a = \sqrt{2} \ 120 \sin(\omega t)$ V
- $v_b = \sqrt{2} \ 120 \sin(\omega t + 120^\circ)$ V
- $v_c = \sqrt{2} \ 120 \sin(\omega t - 120^\circ)$ V
- $\omega = 2\pi f; f = 60$ Hz
- $R = 10\Omega$

- Calculate the amplitude of the output voltage and current.
- Simulate the circuit in Fig. 2 using PSIM and plot the output voltage, output current and the current in each diode.
- Explain what you observe from the waveforms. What diodes are conducting at each portion of time? What is the conduction angle for the diodes? Explain why.

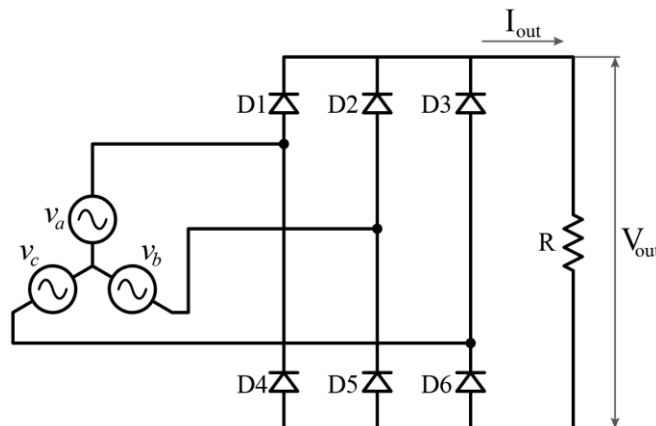


Fig 3 - Three Phase Rectifier

- 4) The circuit shown in Fig. 4 is often used to control the brightness of Light Emitting Diodes (LEDs) by using PWM modulation using a digital microcontroller. An LED works as a rectifier diode, and the LED brightness is proportional to the average current that passes through the diode (i_D).

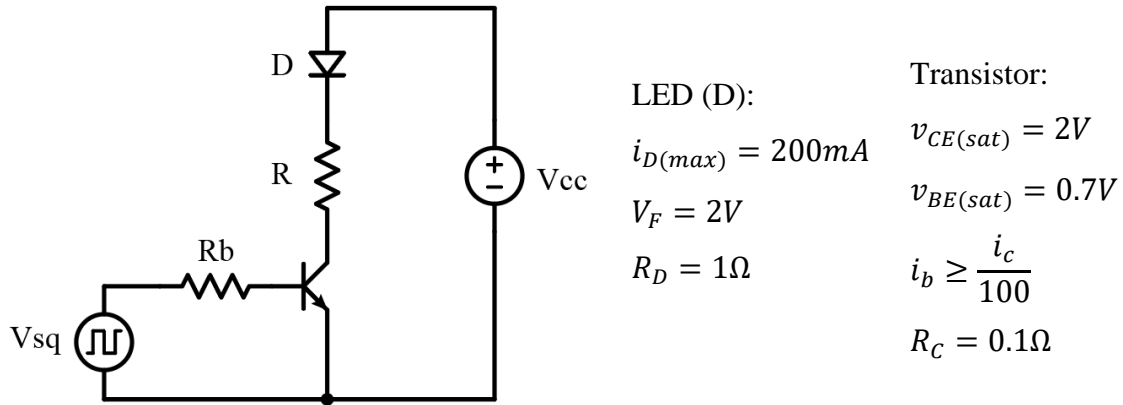


Fig 4 – LED driver circuit

V_{sq} is a square waveform (digital microcontroller output) that alternates between 0V and 5V, at a frequency of 1kHz. The proportion of time in which V_{sq} stays high can be adjusted to change the brightness.

- a) For $V_{cc} = 5V$, calculate:
- The value of the resistor R necessary to achieve full brightness when the transistor stays ON continuously
 - The maximum value of the resistor R_b that enables such condition
 - The average diode power (P_D), resistor power (P_R), transistor power (P_T), and the source power ($P_{V_{cc}}$) for a brightness of 50%.
- b) Repeat all calculations performed in a), in this case for $V_{cc} = 12V$